

Name - Sumit Kumar (G21921)

Class - B.Tech (CSE)

Uni. roll no. - 2000213 (B3)

Sem. - 2nd (MST-18t)

Subject - Basic Electrical & Electronics Engineering.

Subject code - (ACEE-101)

### Section-A

Q1.

(i) Ans:- Active element :- Elements which can perform the operation of circuit independently.  
e.g. - diodes, transistors.

Passive element :- which are not able to perform the operation of circuit independently.  
e.g. - R, L, C.

(ii) Ans:- It states that the electric current flowing through a conductor is directly proportional to the potential difference applied across its two terminals when the temperature and other atmospheric conditions remain unchanged.

$$V \propto I$$

$$V = IR$$

Where R is Constant of proportionality called Resistance.

Limitations:-

- (i) It is applicable only for DC circuits.
- (ii) Not valid if the atmospheric conditions are changed.
- (iii) not applicable for semiconductor devices.

(2)

(iii) Ans 1-

RMS value :  $\rightarrow$  effective value or virtual value  
 is the rms value of an alternating current  
 is the value of that direct current which  
 produces the same amount of heat flowing  
 through a conductor for a give time as  
 produced by the ~~current~~ alternating current  
 when flowing through the same conductor  
 for a same time.

Average value :  $\rightarrow$  It is the value of that direct  
 current which transfers across any circuit the  
 same amount of charge as is transferred by  
 the alternating current where the two half  
 cycles are exactly similar the average value  
 over a complete cycle is zero.

Form factor :  $\rightarrow$  The ratio of rms value or average  
 value is called form factor. It is  
 denoted by  $k_f$ .

$$k_f = \frac{\text{Rms value}}{\text{avg value}}$$

$$k_f = \frac{I_{\text{rms}}}{I_{\text{av}}} = \frac{I_{\text{max}}/\sqrt{2}}{2 I_{\text{max}}/\pi}$$

$$k_f = 1.11$$

(3)

Amplitude factor: → The ratio of maximum value to r.m.s. value of an alternating quantity is called Amplitude factor or peak factor.

$$\text{peak factor} = \frac{I_{\max}}{I_{\text{r.m.s}}} \quad \text{or,} \quad \frac{E_{\max}}{E_{\text{r.m.s}}}$$

$$\text{peak factor} = \frac{I_{\max}}{\frac{I_{\max}}{\sqrt{2}}} = \sqrt{2} = 1.414$$

(iv) Sol:-

$$\text{loop I} - 12 = 12I_1 + 10(I_1 - I_2) \quad \text{--- (i)}$$

$$\text{loop II} - 10 = 6I_2 + 10(I_1 + I_2) \quad \text{--- (ii)}$$

Note  
from eqn (i),

$$12 = 12I_1 + 10I_1 - 10I_2$$

$$12 = 22I_1 - 10I_2 \quad \text{--- (iii)}$$

from eqn (ii),

$$10 = 6I_2 + 10I_1 + 10I_2$$

$$10 = 10I_1 + 16I_2 \quad \text{--- (iv)}$$

from eqn (iii) & (iv),

$$12 = 22I_1 - 10I_2$$

$$10 = 16I_2 + 10I_1$$

$$\underline{32 = 38I_2}$$

$$I_2 = \frac{32}{38} \approx 0.842 \text{ A}$$

eqn (i)

$$12 = 22I_1 - 10I_2$$

$$12 = 22I_1 - 10 \times 0.842$$

$$12 = 22I_1 - 8.42$$

$$12 + 8.42 = 22I_1$$

(4)

$$20.42 = 22 I_1$$

$$I_1 = \frac{20.42}{22} = 0.928 \text{ A}$$

$$\therefore \text{Current in } 10\Omega = I_1 + I_2$$

$$= 0.928 + 0.842$$

$$\Rightarrow 1 + 1 = 2 \text{ A} \quad \underline{\text{Ans}}$$

(V) Ans 1 - Electrical Energy:  $\rightarrow$  It is the total amount of work done in an Electrical circuit.  
Its unit watt hour.

$$W = VIt$$

Mechanical Energy:  $\rightarrow$  when a body to which force is applied moves in or opposite direction of the applied force, work is said to be done by or against the body. The unit of work is Newton metre or Joule.


$$W = F \times S$$

$$\text{One unit} = 3.6 \times 10^6 \text{ watt.sec}$$

(5)

Section-B

Q2. (i) Ans →

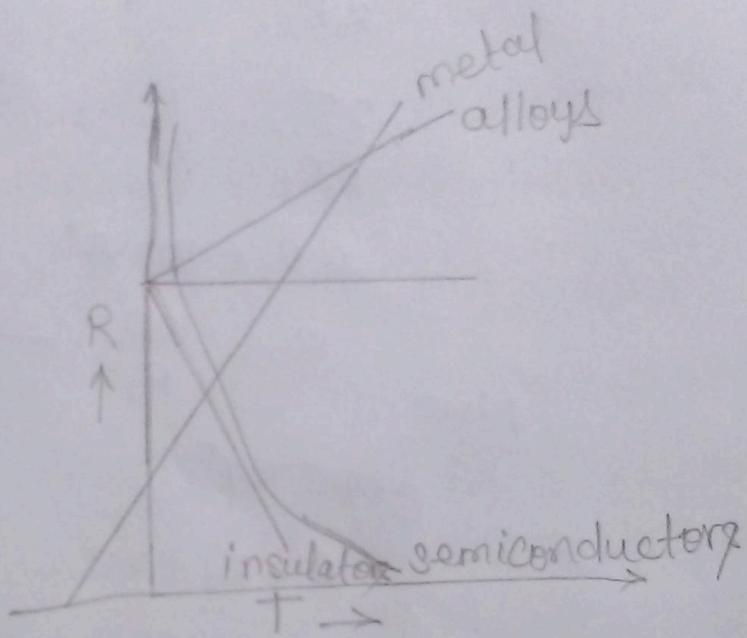

- (a) for pure metals:  $\rightarrow$  As the temperature increases, resistance also increases and  $\alpha$  is positive.
- (b) For insulators, Semiconductors and electrolytes:  $\rightarrow$  As temperature increases, resistance decreases and  $\alpha$  is -ve.
- (c) For alloys:  $\rightarrow$  As temperature increases, there is small increase in resistance and  $\alpha$  has very small positive value.

(6)

Q2.

Given that

$$(i) \text{ Ans} 1 - R_1 + R_2 = 25\Omega \quad \text{--- (i)}$$

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{4} \Omega$$

Then

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{4} \Omega$$

$$\frac{R_2 + R_1}{R_1 R_2} = \frac{1}{4}$$

$$\frac{25}{R_1 R_2} = \frac{1}{4}$$

$$R_1 R_2 = 100 \Omega$$

$$R_2 = \frac{100}{R_1} \quad \text{--- (ii)}$$

Now

from eqn (i)

$$R_1 + R_2 = 25\Omega$$

$$R_1 + \frac{100}{R_1} = 25 \quad \left[ \because R_2 = \frac{100}{R_1} \right]$$

$$R_1^2 + 100 = 25R_1$$

$$R_1^2 - 25R_1 + 100 = 0$$

$$R_1^2 - 20R_1 - 5R_1 + 100 = 0$$

$$R_1(R_1 - 20) - 5(R_1 - 20) = 0$$

$$(R_1 - 5)(R_1 - 20) = 0$$

$$R_1 = 5 \text{ or } 20\Omega$$

Then from eqn (ii)

$$R_2 = \frac{100}{R_1} = \frac{100}{5} = 20\Omega$$

$$R_2 = \frac{100}{R_1} = \frac{100}{20} = 5\Omega$$

(7)

Q3. Sol<sup>n</sup>- Let  $R_0$  → is the resistance of any material at  $0^\circ\text{C}$  and  $R_t$  → resistance at  $t^\circ\text{C}$  then change at  $0^\circ\text{C}$ ,  $R = R_0$ ,  $\alpha = \alpha_0$   
 at  $t_1^\circ\text{C}$ ,  $R = R_1$ ,  $\alpha = \alpha_1$   
 According to definition

$$R_1 - R_0 = \alpha_0 R_0 (t_1 - 0)$$

$$R_1 - R_0 = \alpha_0 R_0 t \quad \dots \textcircled{1}$$

$$R_1 = R_0 (1 + \alpha_0 t_1)$$

Let the resistance  $R_1$  at  $t_1^\circ\text{C}$  be now reduced to  $0^\circ\text{C}$  and gives value  $R_0$

$$R_0 = R_1 [1 + \alpha_1 (0 - t_1)]$$

$$R_0 = R_1 [1 - \alpha_1 t_1] \quad \dots \textcircled{2}$$

$$R_0 = R_1 - R_1 \alpha_1 t_1$$

$$\alpha_1 = \frac{R_1 - R_0}{R_1 t_1} \quad \dots \textcircled{3}$$

Put  $\textcircled{1}$  in  $\textcircled{3}$

$$\alpha_1 = \frac{\alpha_0 R_0 t_1}{R_1 t_1}$$


$$\alpha_1 = \alpha_0 \frac{R_0}{R_0 (1 + \alpha_0 t_1)}$$

$$\alpha_1 = \frac{\alpha_0}{(1 + \alpha_0 t_1)}$$

Hence, Required Eq<sup>n</sup>.

Q4. Soln:-  $\Delta \rightarrow Y$

(8)

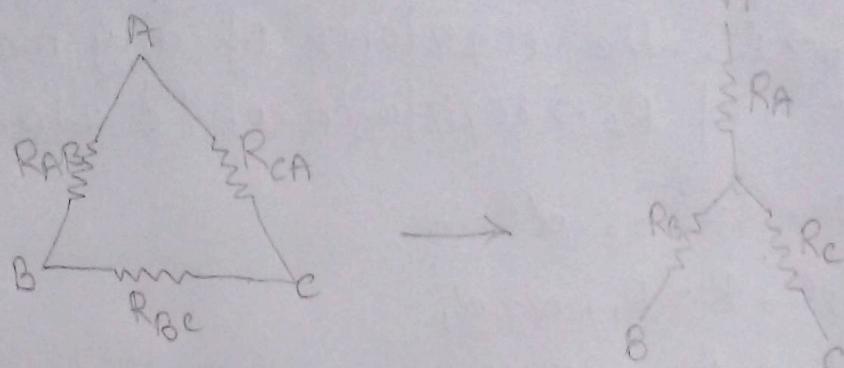

The equivalent resistance across terminals A and B,  $R_{AB}$  of star =  $R_{AB}$  of Delta.

$$R_A + R_B = \frac{R_{AB} (R_{BC} + R_{CA})}{R_{AB} + (R_{BC} + R_{CA})} \quad \text{--- (1)}$$

likewise  $R_B + R_C = \frac{R_{BC} (R_{AB} + R_{CA})}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (2)}$

likewise  $R_C + R_A = \frac{R_{CA} (R_{AB} + R_{BC})}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (3)}$

Subtract (2) from (1) and add the result to (3)

$$(1) - (2) \quad R_A + R_B - R_B - R_C = \frac{R_{AB} (R_{BC} + R_{CA}) - R_{BC} (R_{AB} + R_{CA})}{R_{AB} + R_{BC} + R_{CA}}$$

$$R_A - R_C = \frac{(R_{AB} - R_{BC}) R_{CA}}{R_{AB} + R_{BC} + R_{CA}}$$

$$R_A - R_C = \frac{R_{AB} R_{CA} - R_{BC} R_{CA}}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (4)}$$

$$(4) + (3), \quad R_A + R_C + R_C + R_A = \frac{R_{AB} R_{CA} - R_{BC} R_{CA}}{R_{AB} + R_{BC} + R_{CA}} + \frac{R_{BC} R_{AB} + R_{CA} R_{BC}}{R_{AB} + R_{BC} + R_{CA}}$$

(g)

$$R_A = \frac{R_{BC} \cdot \frac{R_A^2}{R_c R_B} \cdot R_{BC}}{R_{BC} \left( \frac{R_A}{R_c} + 1 + \frac{R_A}{R_B} \right)}$$

$$\Rightarrow R_A \left( \frac{R_A}{R_c} + 1 + \frac{R_A}{R_B} \right) = \frac{R_A^2}{R_c R_B} \cdot R_{BC}$$

$$\Rightarrow \frac{R_A R_B + R_c R_B + R_A R_c}{R_c R_B} = \frac{R_A}{R_c R_B} \cdot R_{BC}$$

$$\boxed{\frac{R_A R_B + R_c R_B + R_A R_c}{R_A} = R_{BC}}$$

Similarly,



$$\boxed{R_{AB} = \frac{R_A R_B + R_B R_c + R_c R_A}{R_c}}$$

Similarly,

$$\boxed{R_{CA} = \frac{R_A R_B + R_B R_c + R_c R_A}{R_B}}$$

Q.S. Ans 1 - Transducers : It is a device with converts any physical quantity like temperature, pressure, displacement, flow, vibrations, humidity, force etc into an equivalent electrical signal in the form of voltage or current.

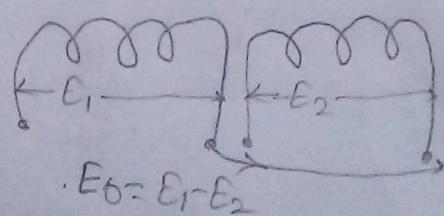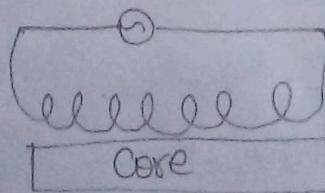LVDT = (Linear variable differential Transducer) :-



$$2R_A = \frac{2R_{AB}R_{CA}}{R_{AB}+R_{BC}+R_{CA}}$$

$$R_A = \frac{R_{AB}R_{CA}}{R_{AB}+R_{BC}+R_{CA}} \quad \text{--- (5)}$$

Similarly,

$$R_B = \frac{R_{BC}R_{AB}}{R_{AB}+R_{BC}+R_{CA}} \quad \text{--- (6)}$$

Similarly,

$$R_C = \frac{R_{BC}R_{CA}}{R_{AB}+R_{BC}+R_{CA}} \quad \text{--- (7)}$$

(2) from  $\Delta \rightarrow \Delta$

Divide (5) by (6)

$$\frac{R_A}{R_B} = \frac{R_{AB}R_{CA}}{R_{BC}R_{AB}} = \frac{R_{CA}}{R_{BC}}$$

$$R_{CA} = \frac{R_A}{R_B} \cdot R_{BC} \quad \text{--- (8)}$$

Divide (5) by (7)

$$\frac{R_A}{R_C} = \frac{R_{AB}}{R_{BC}}$$

$$R_{AB} = \frac{R_A}{R_C} \cdot R_{BC} \quad \text{--- (9)}$$

put (8) & (9) in (5)

$$R_A = \frac{\left(\frac{R_A}{R_C} \cdot R_{BC}\right) \cdot \left(\frac{R_A}{R_B} \cdot R_{BC}\right)}{\frac{R_A}{R_C} \cdot R_{BC} + R_{BC} + \frac{R_A}{R_B} \cdot R_{BC}}$$

Construction :-

- (i) It consists of one primary.
- (ii) secondary windings around as a cylindrical coil with rod shaped core positioned inside the coil. The rod shaped core provides low reluctance path for the flux linking with coil.
- (iii) Displacement of moving core is to be measured.

Working :-

- (i) Connect primary winding to AC Supply Source.
- (ii) Assume the core is at centre of the coils.  
Therefore the flux linking with both secondaries will be equal. Hence due to equal flux linkage.  
 $E_1 = E_2$  and  $E_o = E_1 - E_2 = 0$ . This position of core is called as null position.
- (iii) Now If the core is displaced towards Secondary one then the flux linking with Secondary one increases and Secondary two decreases.  
 $E_1 > E_2$  and  $E_o = \text{positive}$ .
- (iv) Similarly If the core is displaced towards Secondary two then the flux linking with Secondary two increase and Secondary ~~one~~  
~~increase~~ two decrease  $E_1 < E_2$  and  $E_o$  is negative.